

HOME TASK

Aim :

The LED should turn on and off by alternating button presses

Circuit diagram:

