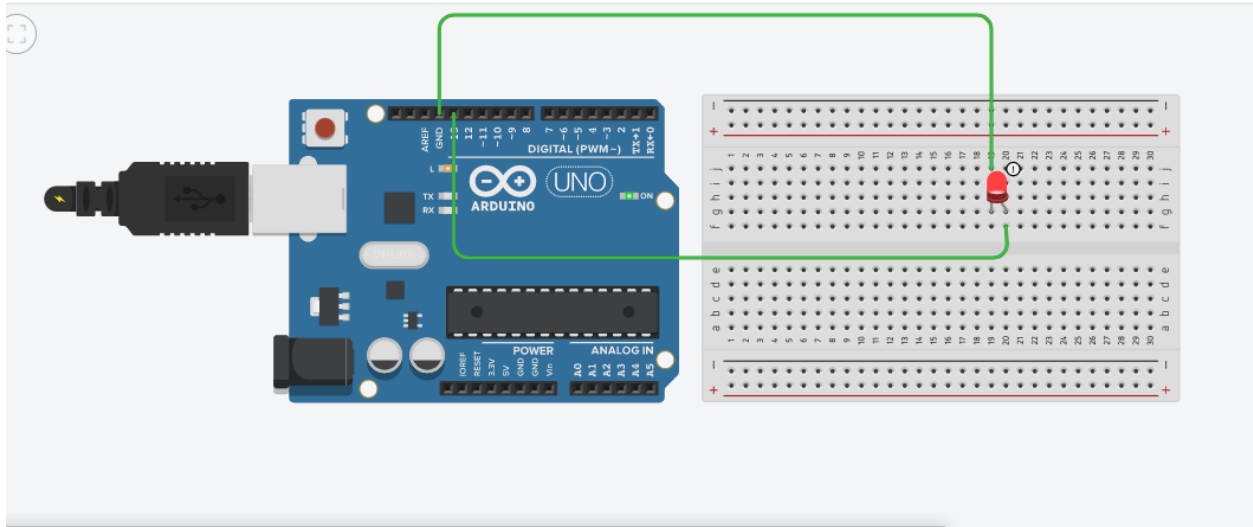


---

# Experiment 1

## DESIGN AN LED FLASHER

### Circuit Diagram:



### Theory:

#### CONCEPT USED:

- By using kirchoff's voltage law  
&
- By using kirchoff's current law

#### LEARNING AND OBSERVATIONS:

- Connections in Breadboard and wiring.
- How to control arduino and its coding.
- Use of multimeter for continuity.

## **OBSERVATION:**

- **Blinking of an LED.**
- **Relation between software and hardware.**

## **PROBLEMS & TROUBLESHOOTING:**

- **To select the right port and type of arduino**
- **To check the loose connections**
- **To check the connections according to the codes**
- **To check the continuity of the circuit**
- **To check the flow of current in the circuit**

## **PRECAUTIONS:**

- **Handle tools carefully**
- **Wear gloves**
- **Do not connect arduino till the circuit is complete**

## **OUTCOMES:**

- **On and off of an LED**
- **Used in project works**

**Created By-**

**Rishabh Anand**  
**19BCS4525**  
**CSE-IoT (1A)**  
**CHANDIGARH UNIVERSITY**